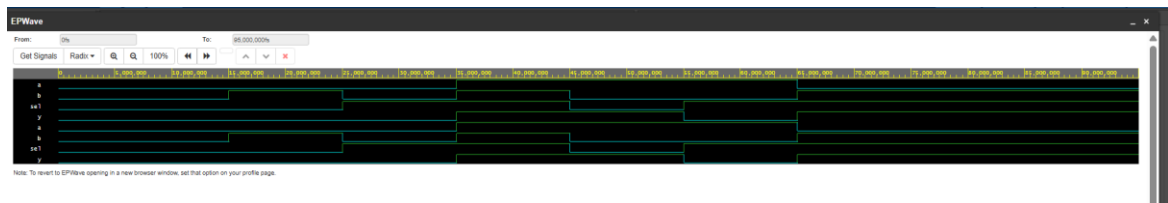
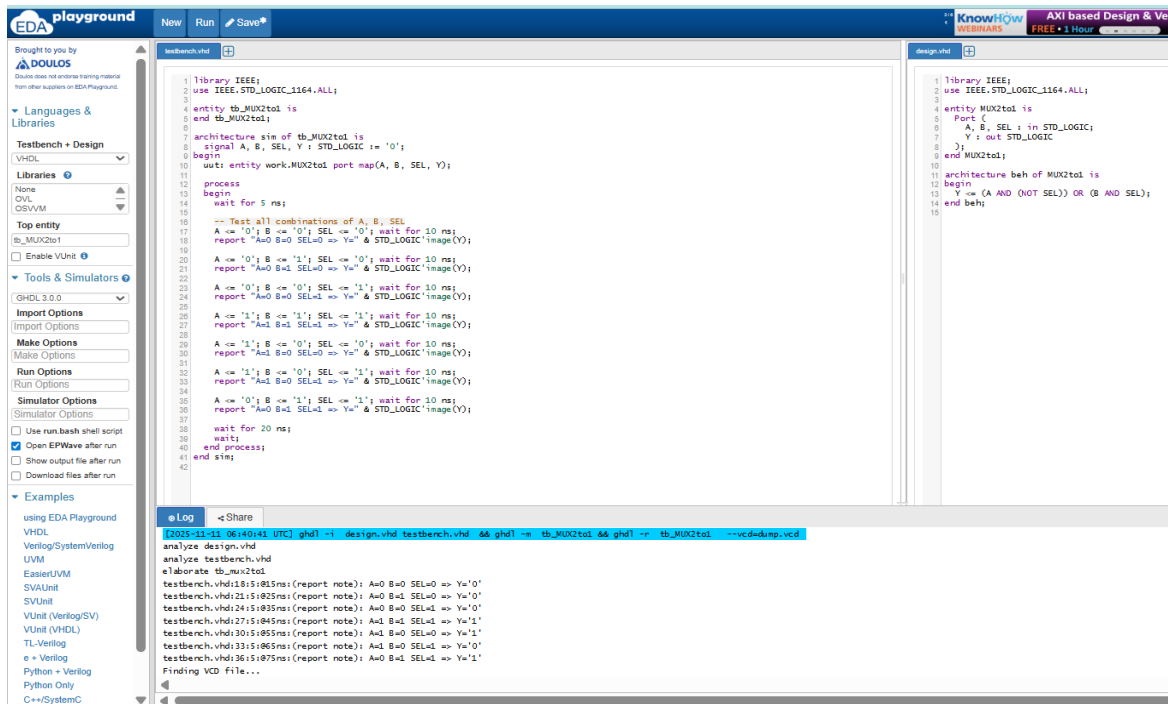


## VHDL 7: WRITE A VHDL CODE FOR MULTIPLEXER.



## VHDL 8: WRITE A VHDL CODE FOR DECODER.

